

22213

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) State the typical knee voltage values for Si and Ge diodes.
- b) State the need of rectifiers. List the types of rectifiers.
- c) Draw a symbol of PNP and NPN transistors.
- d) State the output voltage of IC 7824 and IC 7906.
- e) Suggest the suitable diode type for voltage regulator circuit.
- f) Define the terms
- i) Line Regulation
- ii) Load Regulation
- g) Draw the symbol and truth table of EX-OR gate.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Describe the V-I characteristics of a P-N junction diode with proper sketch and define
 - i) Break over voltage
 - ii) Reverse breakdown voltage
 - b) Describe the working of half wave rectifier with LC filter using neat circuit diagram
 - c) Explain transistor as a switch with neat sketch.
 - d) Sketch the block diagram of DC regulated power supply. State the function of each block.
- 3. Attempt any THREE of the following:** **12**
- a) Explain the functional block diagram of IC723 with neat sketch.
 - b) Describe the working of crystal oscillator with neat diagram.
 - c) State the various transistor configurations. State any four applications of BJT.
 - d) Compare half-wave rectifier with full wave centre-tapped rectifier on the basis of Ripple factor, Rectifier efficiency, TUF and PIV.
- 4. Attempt any THREE of the following:** **12**
- a) State the Barkhausen criteria. Draw the circuit diagram of colpitt's oscillator.
 - b) Draw the circuit diagram of bridge rectifier with π filter. Draw its input and output waveforms.
 - c) A transistor has $I_B = 110\mu\text{A}$, $I_C = 2\text{mA}$. Calculate α and β .
 - d) Describe the construction details of light emitting diode (LED) with neat sketch. State the application of LED.

- e) Figure No. 01. shows the centre tapped full wave rectifier circuit. Assume both the diodes to be ideal. Determine
- DC output voltage (V_{dc}) and
 - Peak inverse voltage (PIV) of diode

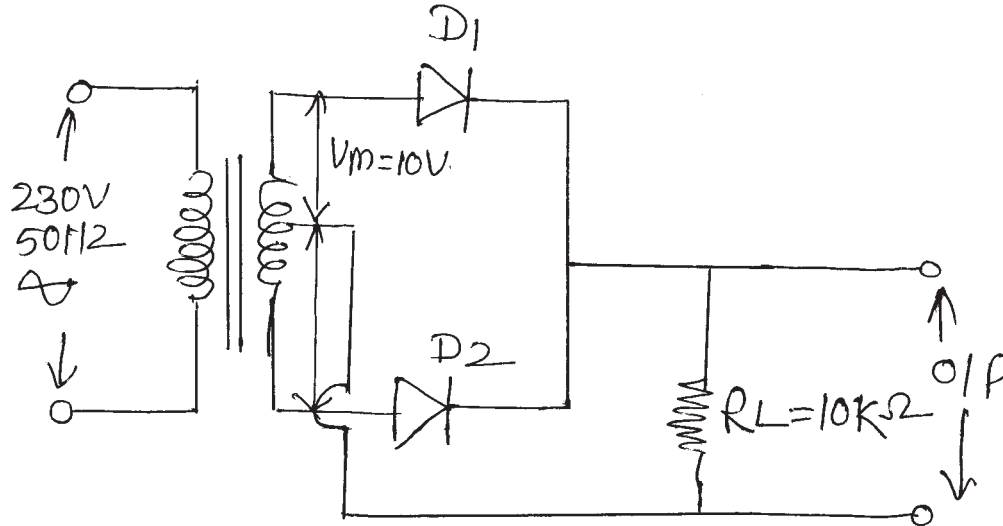


Figure No. 01.

5. Attempt any TWO of the following:

12

- A transistor has a typical $\beta = 100$. If the collector current is 40mA. Determine the value of base current, emitter current and α .
- For zener voltage regulator, if $I_{Zmin} = 2\text{mA}$, $I_{Zmax} = 20\text{mA}$, $V_Z = 4.7\text{V}$. Determine the range of input voltage over which output voltage remains constant. $R_L = 1\text{k}\Omega$, $R = 1\Omega$, $Z_Z = 0\Omega$. Refer Figure No. 02.

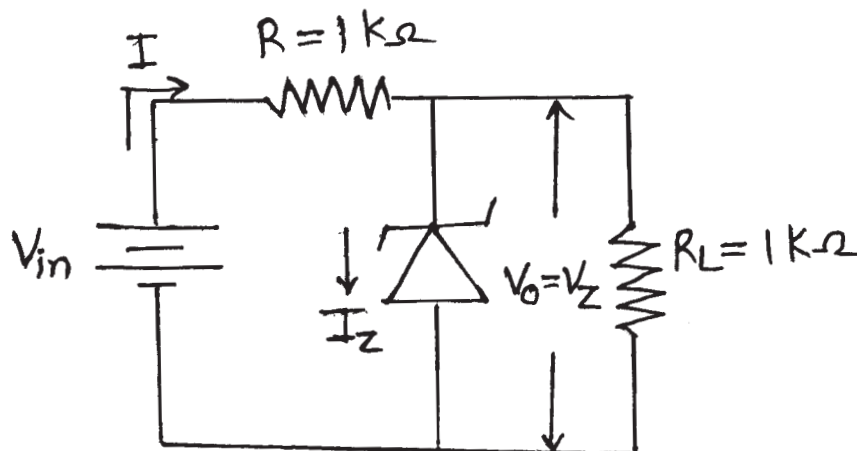


Figure No. 02.

P.T.O.

- c) State the disadvantage of JK flip-flop. Explain the working of MS JK flip-flop with proper diagram.

6. Attempt any TWO of the following:

12

- a) Compare RC and LC oscillators. (six points)
- b) Sketch common base configuration input characteristics for two different values of V_{CB} and O/P characteristics for two different values I_E . Write the formula for input resistance and output resistance.
- c) Convert the following
- i) $(208)_{10} = (\quad)_2$
 - ii) $(AgC)_{16} = (\quad)_8$
 - iii) $(247)_8 = (\quad)_{10}$
-