

22213

22223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

- 1. Attempt any FIVE of the following **10****
- a) Draw the symbol of LED and PN junction diode.
 - b) Name the circuit to obtain D.C. signal from A.C. signal.
 - c) State relation between emitter current (I_E) base current (I_B) and collector current (I_C) of BJT.
 - d) Draw pin configuration of IC723.
 - e) List any two applications of zener diode.
 - f) Write three terminal voltage regulator IC for obtaining :
 - i) +5V
 - ii) -12V
 - g) Draw symbol and write truth table of EX-OR gate.

P.T.O.

- 2. Attempt any THREE of the following** **12**
- a) Draw and explain V-I characteristics of PN junction diode.
 - b) Explain center tapped full wave rectifier with the help of circuit diagram and draw input, output waveforms.
 - c) Compare CB, CE and CC configuration (Any four points)
 - d) Explain with circuit diagram operation of zener diode as a voltage regulator.
- 3. Attempt any THREE of the following** **12**
- a) Draw the block diagram of regulated DC power supply and explain the function of each block.
 - b) Sketch circuit diagram of Hartely oscillator. State expression for frequency of oscillation.
 - c) Describe transistor as a switch with neat sketch.
 - d) In full wave bridge rectifier $V_m = 10V$, $R_L = 10K\Omega$. Find out V_{DC} , I_{DC} , ripple factor and PIV.
- 4. Attempt any THREE of the following** **12**
- a) Compare positive and negative feedback (Any four points).
 - b) Draw the circuit diagram of bridge rectifier with π filter. Draw its input and output waveform.
 - c) In a common base connection, current amplification factor (α) is 0.9. If the emitter current is I_{MA} , determine the value of base current and collector current.
 - d) Describe the working principle of photodiode with proper diagram.
 - e) Name the type of rectifier for each of following feature:
 - i) Highest rectifier efficiency
 - ii) Highest form factor
 - iii) Two diode rectifier circuit
 - iv) $PIV = 2V_m$.

5. Attempt any TWO of the following**12**

- a) Define α and β of transistor and derive the relation between them.
- b) Construct a dual regulated power supply capable of giving $\pm 12V$ using 78XX and 79XX IC'S.
- c) Implement the fundamental logic gates 'OR' gate, 'AND' gate, 'NOT' gate using only NAND gates.

6. Attempt any TWO of the following**12**

- a) Sketch circuit diagram of RC phase shift oscillator. If the value of capacitor. $C = C_1 = C_2 = C_3 = 5\text{pf}$ and frequency of oscillation is 800Hz, calculate value of resistor R_1 ($R = R_1 = R_2 = R_3$).
 - b) Draw output characteristics of common emitter (CE) configuration and explain active, saturation and cut off regions in detail.
 - c) Convert the following numbers:
 - i) $(11010010)_2 = (?)_8$
 - ii) $(109)_{10} = (?)_2$
 - iii) $(6A)_{16} = (?)_{10}$
-