

# 22213

**23124**

**3 Hours / 70 Marks**

Seat No. 

--	--	--	--	--	--	--	--

- 
- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
  - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following: **10****
- a) Draw the symbol of –
    - i) Zener Diode
    - ii) Photo Diode
  - b) Define term Ripple factor for rectifier.
  - c) Draw the symbol of NPN and PNP transistor.
  - d) Define term load regulation.
  - e) List any two applications of Zener diode.
  - f) Name the IC voltage for fixed voltage +5V and –10V.
  - g) Draw the logic symbol and truth table for NAND gate.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) State the working principle of photo diode.
  - b) Explain half-wave rectifier with input-output waveform.
  - c) Describe the working of NPN transistor.
  - d) State the need of D.C. regulated power supply. Also give it's advantages. (any four)
- 3. Attempt any THREE of the following:** **12**
- a) Sketch the block diagram of D.C. regulated power supply. State function of each block.
  - b) List the application of LC and RC oscillators.
  - c) Draw input output characteristics of CE configuration.
  - d) Define filter. Give it's type and draw  $\pi$  type filter.
- 4. Attempt any THREE of the following:** **12**
- a) Compare positive and negative feedback system on the basis of –
    - i) Overall phase shift,
    - ii) Voltage gain,
    - iii) Stability,
    - iv) Application.
  - b) In full wave rectifier  $V_m = 50V$ ,  $R_L = 10 \text{ k}\Omega$ , find  $V_{dc}$ ,  $I_{dc}$  and Ripple factor.
  - c) Describe transistor as switch with neat sketch.
  - d) Explain with diagram construction of LED.
  - e) Draw the circuit diagram of centertap rectifier with LC filter.

- 5. Attempt any TWO of the following:** **12**
- a) Sketch circuit diagram for common base configuration and explain its input and output characteristics.
  - b) Sketch functional block diagram of IC 723 and explain each block in detail.
  - c) Sketch the implementation of OR gate and AND gate using NAND gate.
- 6. Attempt any TWO of the following:** **12**
- a) Define  $\alpha$ ,  $\beta$  and  $\gamma$  of transistor and give relation between  $\alpha$  and  $\beta$  of transistor.
  - b) Convert :-
    - i)  $(416)_{10} = ( )_2$
    - ii)  $(140)_{10} = ( )_{16}$
    - iii)  $(AFC)_{16} = ( )_8$
    - iv)  $(248)_8 = ( )_{10}$
  - c) Sketch colpits oscillator and explain its working. Also state its application.
-